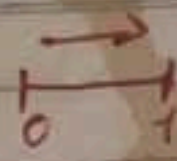


Revisão ED.2




Somadores

★ Meio Somador

		min	Entrada	Saída	
A	B		A B	Soma	Carry
0	0	1	0 0	0	0
0	1	2	0 1	1	0
1	0	3	1 0	1	0
1	1	4	1 1	0	1

$$S = \bar{A}B + A\bar{B}$$

$$S = A \oplus B \quad C = AB$$

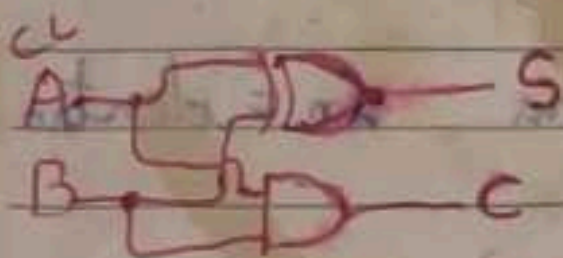

★ Somador Completo

		min	ENTRADA	SAÍDA	
A	B		A B CARRY ENTRADA (TE)	Soma	Carry Saída (TS)
0	0	0	0 0	0	0
0	1	1	0 1	1	0
1	0	2	1 0	1	0
1	1	3	1 1	0	1

Karnaugh S

	B	TE	B
A	0	0	0
A	0	1	0
A	1	0	0
A	1	1	0

Karnaugh TS

Karnaugh TS

	B	TE	B
A	0	0	0
A	0	1	0
A	1	0	0
A	1	1	0

$$TS = ATE + BTE + AB$$

$$TS = TE(A + B) + AB$$

$$TS = (A \oplus B)TE + AB$$

$$S = \bar{A}\bar{B}TE + \bar{A}BTE + A\bar{B}TE + ABTE$$

$$S = A(\bar{B}TE + BTE) + \bar{A}(\bar{B}TE + BTE)$$

$$S = A(B \oplus TE) + \bar{A}(B \oplus TE)$$


$$S = A \oplus B \oplus TE$$

Obs: De Tab. Karnaugh for

N será os termos com



ou exclusivo/XOR "⊕"

EXOR

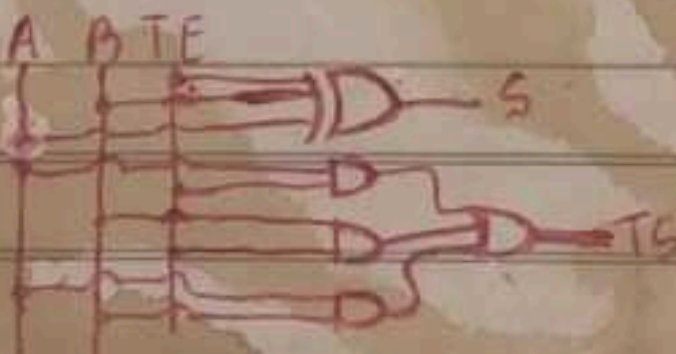

A = 4 bits

B = 4 bits

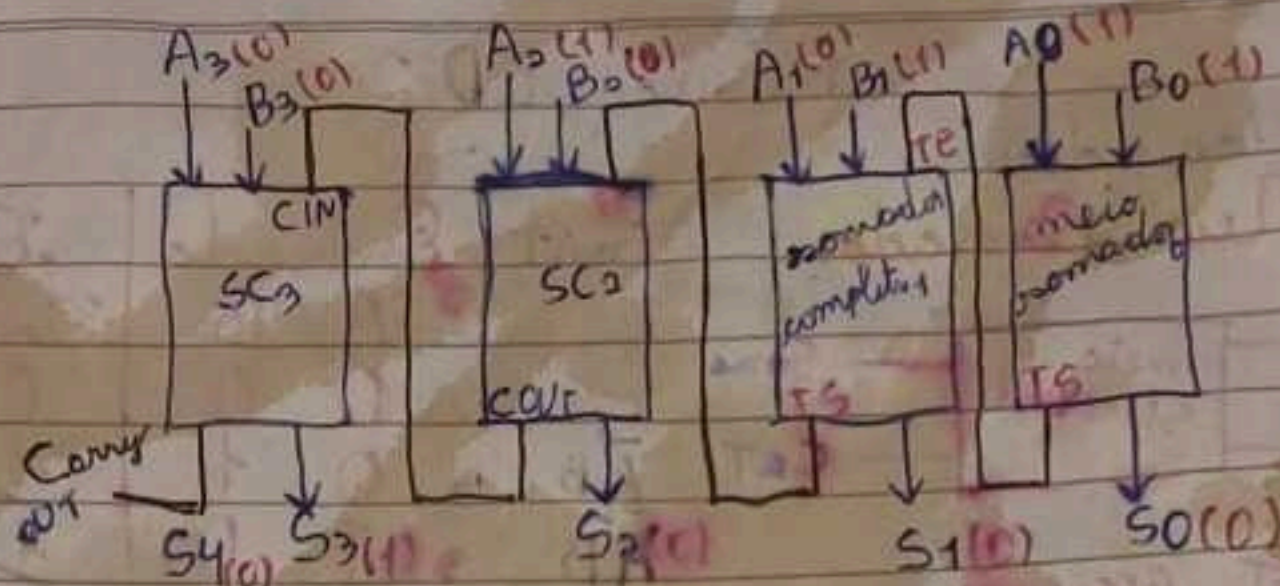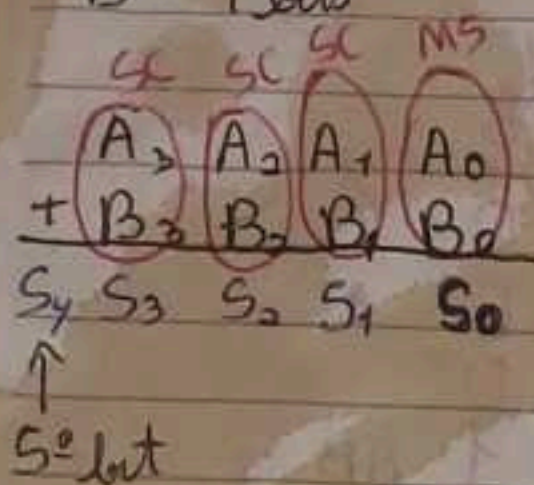

$$\begin{array}{r} A \quad 10101 \\ + B \quad 0011 \\ \hline 1000 \end{array}$$

TS = transporte de saída
TE = transporte de entrada


Obs.: out = fora in = dentro

Booleana SC² para TS

$$TS = \overline{A}BTE + A\overline{B}TE + AB\overline{TE} + ABTE$$

$$TE(\overline{A}B + A\overline{B}) + AB(\overline{TE} + TE)$$

$$TE(A \oplus B) + AB(1)$$

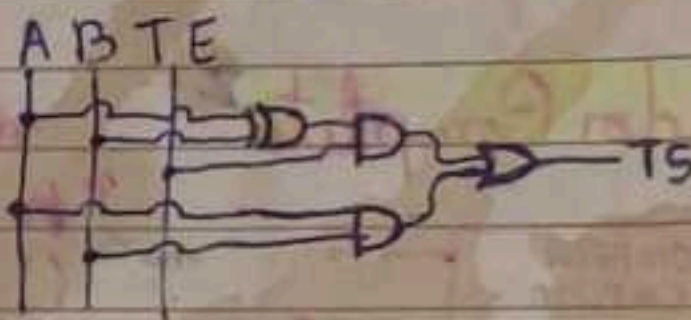


Obs para Booleana

$$\overline{A}(X) + A(\overline{X}) \Rightarrow A \oplus X$$


$$\overline{A}\overline{X} + AX \Rightarrow \overline{A \oplus X} \text{ ou } A \odot X$$

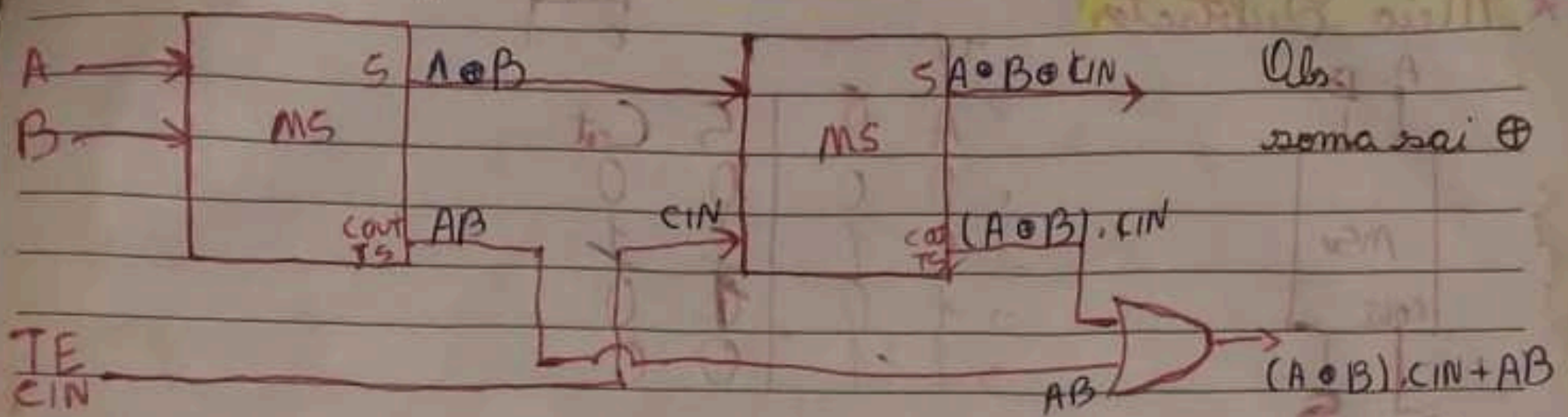Somador completo por meio de meio somadores



Ex: 2 números (A, B) com 2 bits, utilizando apenas meio-somadores.

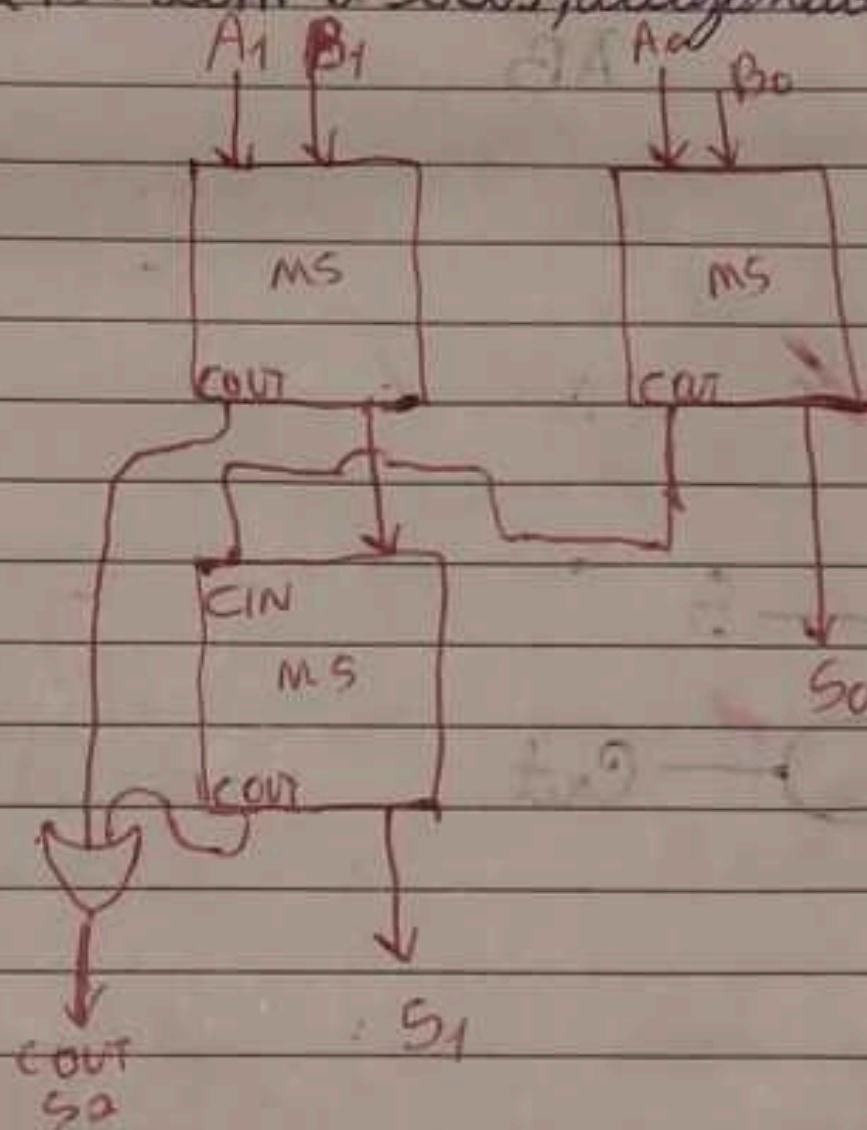$A \rightarrow A_1 A_0$
 $B \rightarrow B_1 B_0$
 $S_2 S_1 S_0$



Se fosse 2 números (A, B) com 5 bits, utilizando apenas meio somadores

FORMULA ED

Seria 9 meio somadores

$$\text{BITS} - 1 = \text{NMS}$$


Portas OR: 4

$$q_{MS} = (\text{NMS} \cdot 2) + 1$$

$$q_{OR} = \text{Bits} - 1$$

Subtratores

* Meio Subtrator

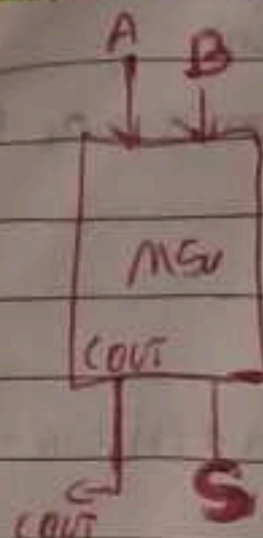

TV			
A	B	S	Cout
0	0	0	0
0	1	1	0
1	0	1	1
1	1	0	1

Booleana S


$$AB + A\bar{B}$$

$$A \oplus B$$


Booleana Cout TS

$$\bar{A}B$$

Circuitos Lógicos

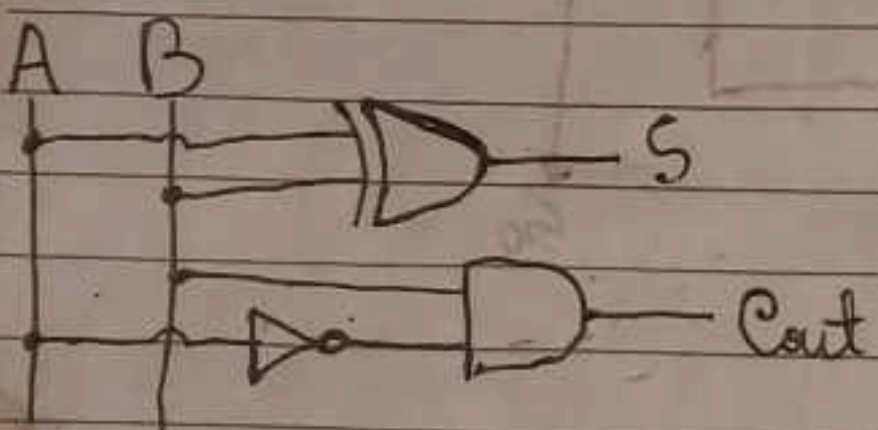

Full Adder Complete

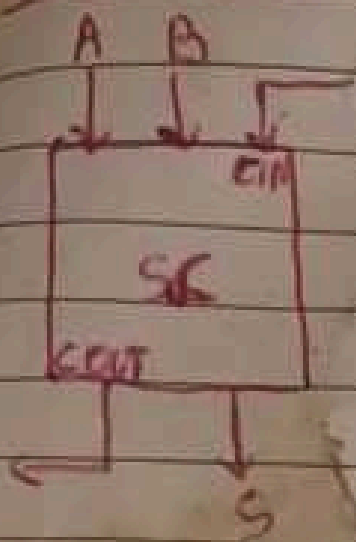

	A	B	Cin	S	Cout
0	0	0	0	0	0
1	0	0	1	1	0
2	0	1	0	1	0
3	0	1	1	0	1
4	1	0	0	1	0
5	1	0	1	0	1
6	1	1	0	0	1
7	1	1	1	1	1



Booleana S

$$S = \bar{A}\bar{B}C_{in} + \bar{A}B\bar{C}_{in} + A\bar{B}\bar{C}_{in} + ABC_{in}$$

$$S = \bar{A}(\bar{B}C_{in} + B\bar{C}_{in}) + A(\bar{B}\bar{C}_{in} + BC_{in})$$

$$S = \bar{A}(B \oplus C_{in}) + A(\bar{B} \oplus C_{in})$$

$$S = A \oplus B \oplus C_{in}$$

→ desnecessário pois tendo mais de dois termos não utilizar Karnaugh

S

	B	B
A	0	1
A	1	0
Cin	Cin	Cin

$$S = A \oplus B \oplus C_{in}$$

Booleana Cout

$$\bar{A}\bar{B}C_{in} + \bar{A}B\bar{C}_{in} + A\bar{B}\bar{C}_{in} + ABC_{in}$$

$$C_{in}(\bar{A}\bar{B} + AB) + \bar{A}B(\bar{C}_{in} + C_{in})$$

$$C_{in}(A \odot B) + \bar{A}B$$

Booleana Cout20

$$\bar{A}\bar{B}C_{in} + \bar{A}B\bar{C}_{in} + A\bar{B}\bar{C}_{in} + ABC_{in}$$

$$\bar{A}(\bar{B}C_{in} + B\bar{C}_{in} + BC_{in}) + AB\bar{C}_{in}$$

$$\bar{A}(\bar{B}C_{in} + B(\bar{C}_{in} + C_{in})) + AB\bar{C}_{in}$$

$$AC_{in} + B + AB\bar{C}_{in}$$

Cout

	B	B
A	0	1
A	0	0
Cin	Cin	Cin

$$Cout = \bar{A}C_{in} + B\bar{C}_{in} + \bar{A}B$$

$$\bar{A}(C_{in} + B) + BC_{in}$$


$$C_{in}(\bar{A} + B) +$$

$$S = A \oplus B \oplus C_{in}$$


$$Cout = (A \oplus B)C_{in} + \bar{A}B$$

números
tratações

Circuito Lógico

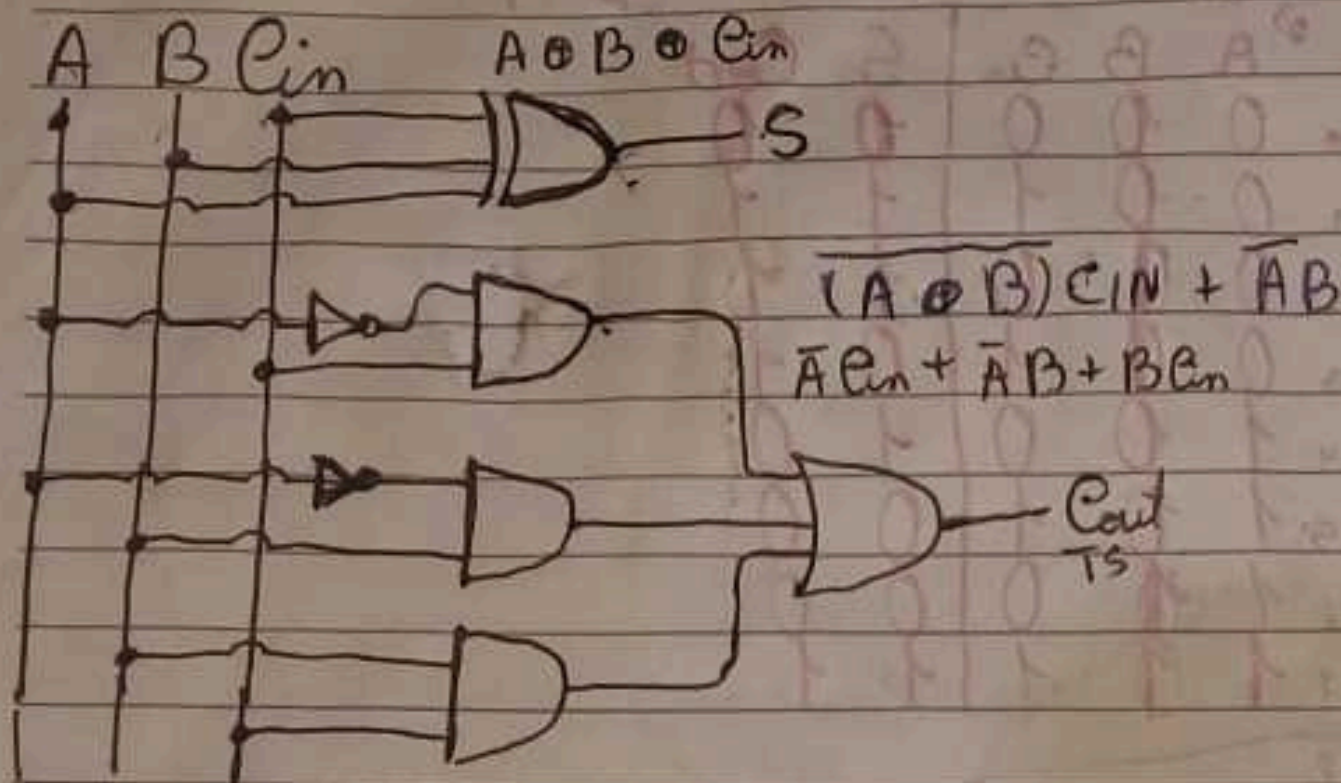


Subtrator completo com meio subtrator

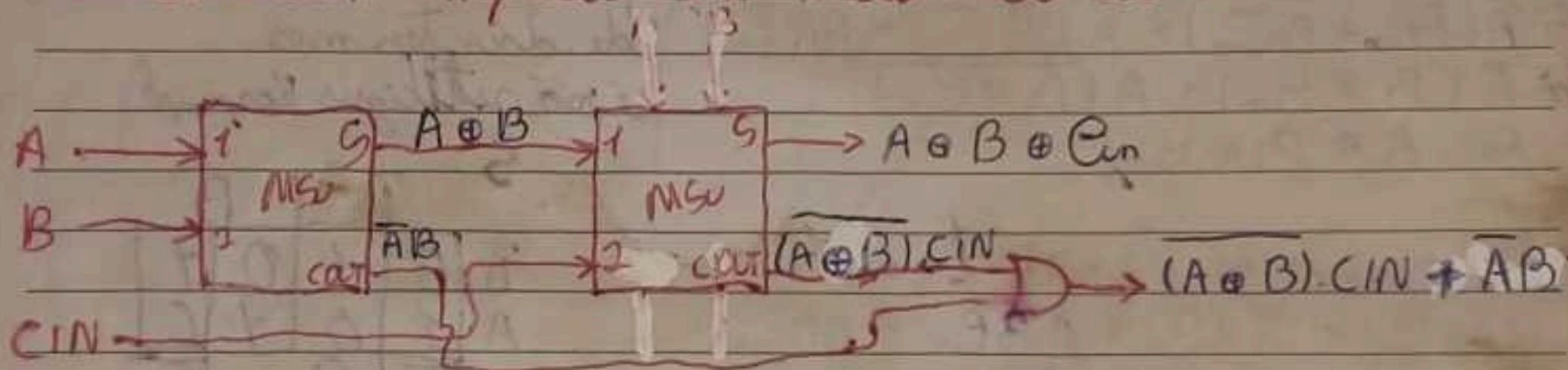


Ex: A e B com 4 bits utilizando meio subtrator e subtrator completo

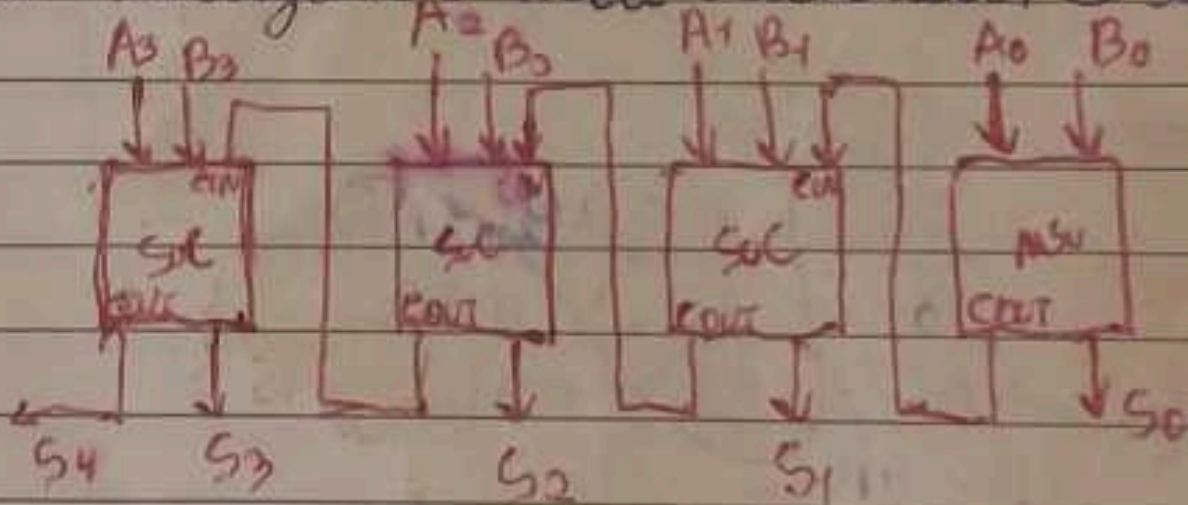
$A_3 A_2 A_1 A_0$
 $- B_3 B_2 B_1 B_0$
 $S_4 S_3 S_2 S_1 S_0$



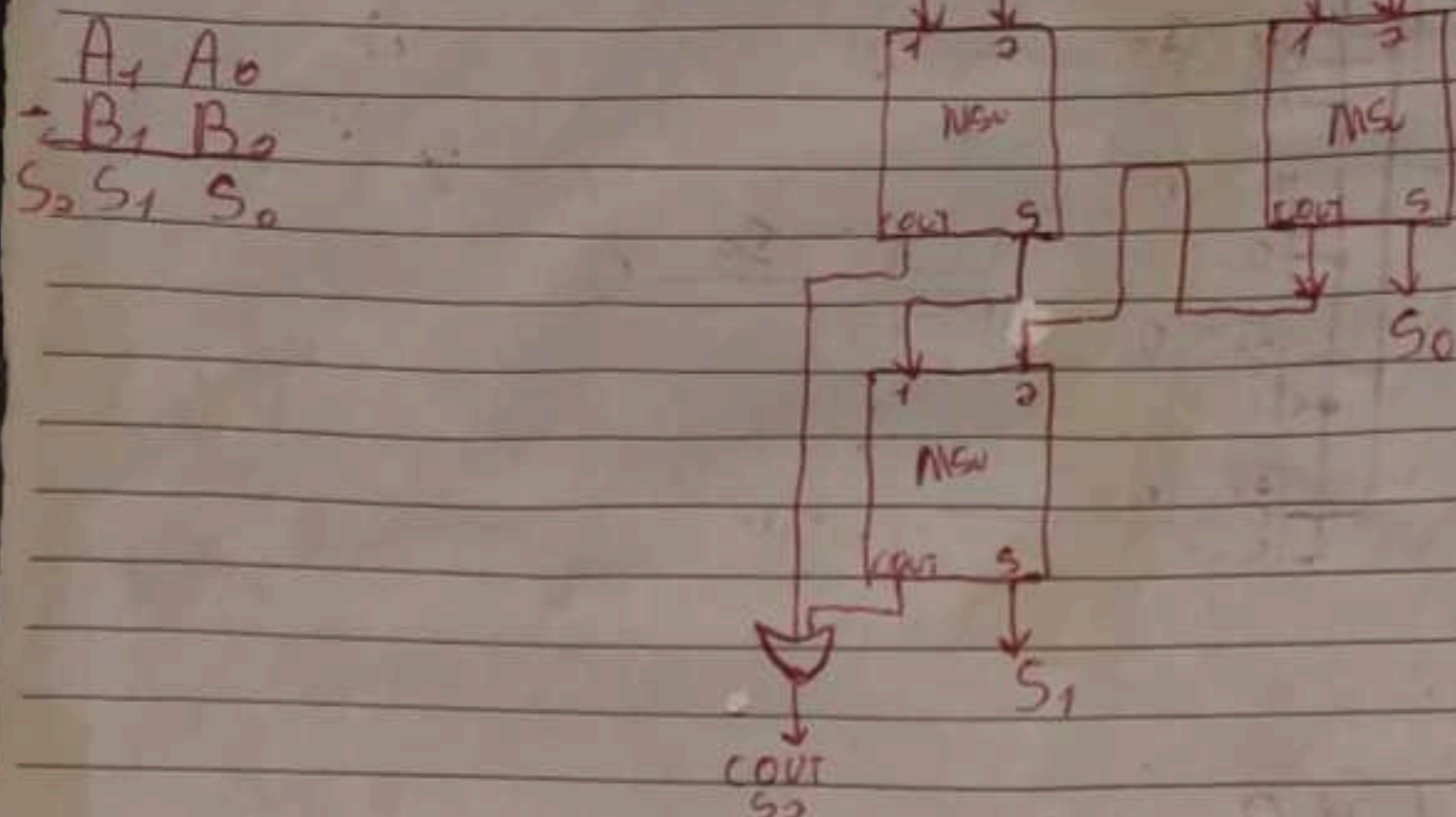
2 números (A e B) com 2 bits utilizando apenas meio sub-
tratores



★ Multiplexers - Demultiplexers

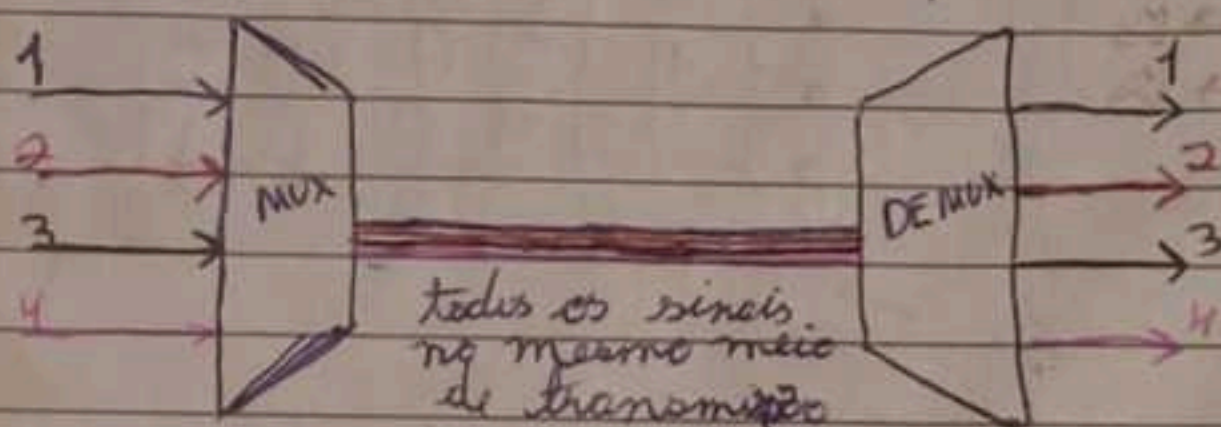

Mux de 4 canais

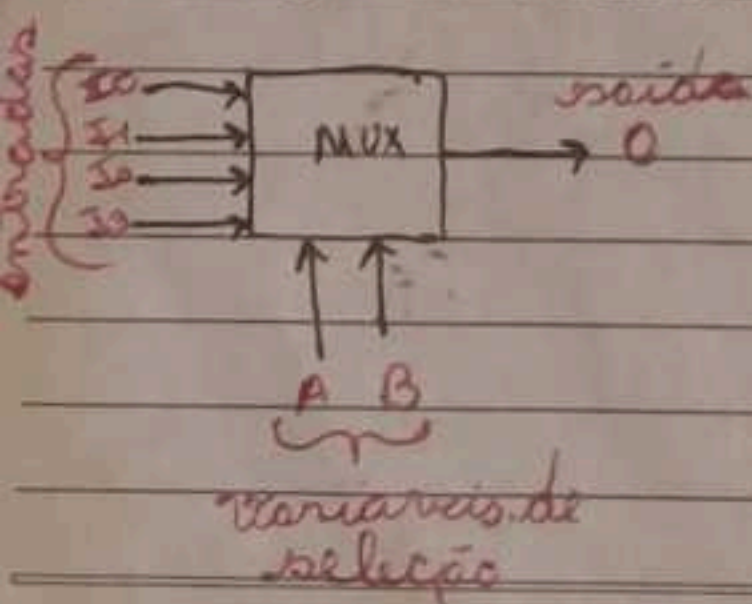


Truth Table for a 4-channel MUX:

	TV		
	A	B	Output
$\bar{A}\bar{B}$	0	0	I_0
$\bar{A}B$	0	1	I_1
$A\bar{B}$	1	0	I_2
AB	1	1	I_3


□ □ □ □ □ □ □

CL

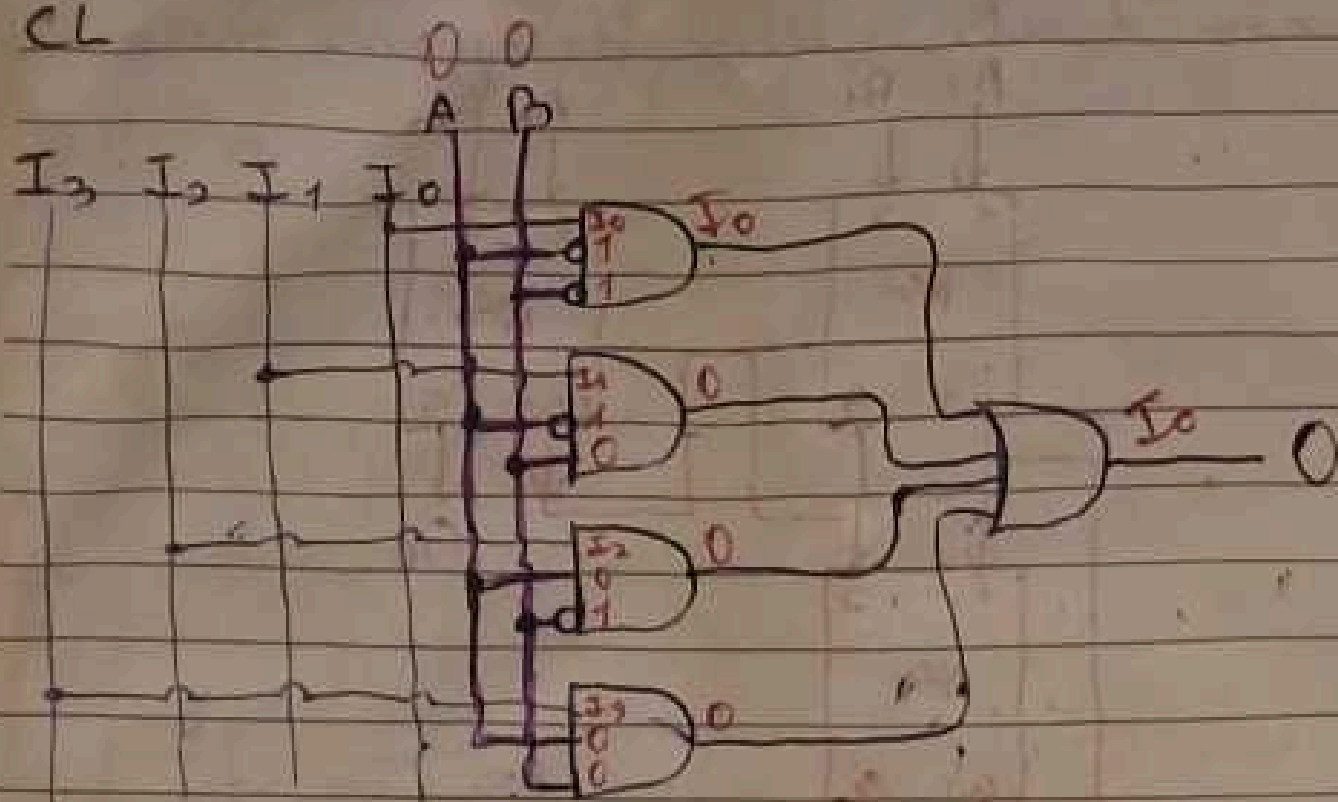

A B

★ DEMUX de 4 Canais:

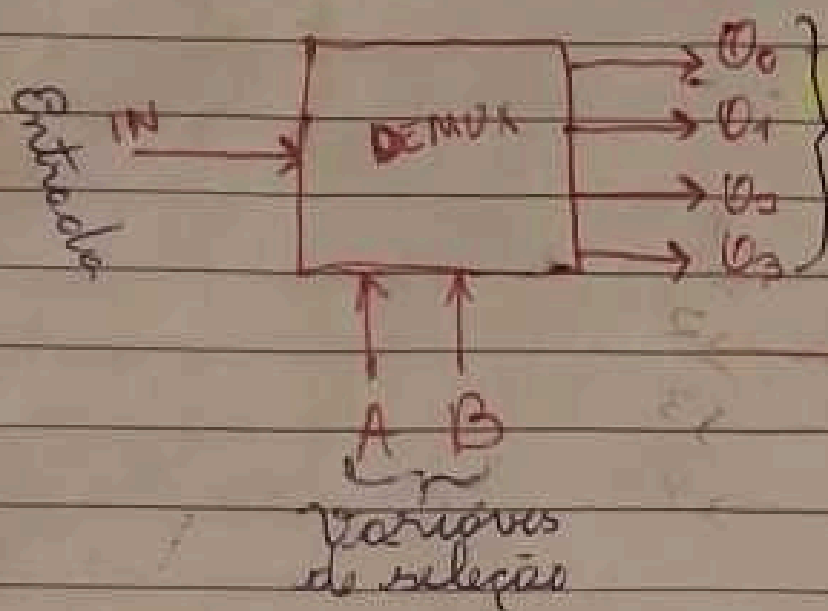

TV					
A	B	U_0	U_1	U_2	U_3
0	0	IN	0	0	0
0	1	0	IN	0	0
1	0	0	0	IN	0
1	1	0	0	0	IN

CL

